

Connect a 4-20mA sensor to the FLX 3401 extension card


1. Purpose

This document explains how to use a 4-20mA sensor with a FLX3401 IO extension card.

The FLX3401 IO extension card has been designed to connect 0-10V sensors. However, through additional wiring and a resistor, you can also connect your 4-20mA sensors on this extension card.

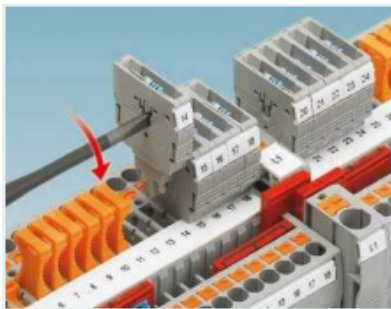
2. Needed materials

- 4 Resistors of **330R, 0.5W** with a good precision, like for example a tolerance of **0.1%**
- To ease the assembly we recommend to use a terminal block like, as for example:
 - Phoenix Contact : component terminal blocks




(https://www.phoenixcontact.com/online/portal/us?ldmy&urle=wcm:path:/usen/web/main/products/subcategory_pages/component_terminal_blocks_p-15-03-01/b7227917-90da-4c40-bcb0-5626dc82d0ba)

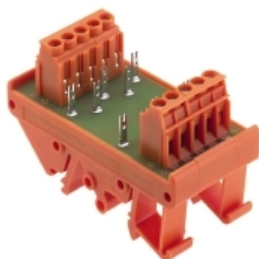- Weidmüller Rectifier modul: RSX Loetst. LP (Reference 329761001)



([http://catalog.weidmueller.com/procat/Product.jsp;jsessionid=76C583DE614DFEC205DDC153C63D500C?productId=\(%5b0329761001%5d\)&page=Product](http://catalog.weidmueller.com/procat/Product.jsp;jsessionid=76C583DE614DFEC205DDC153C63D500C?productId=(%5b0329761001%5d)&page=Product))

3. Wiring diagram

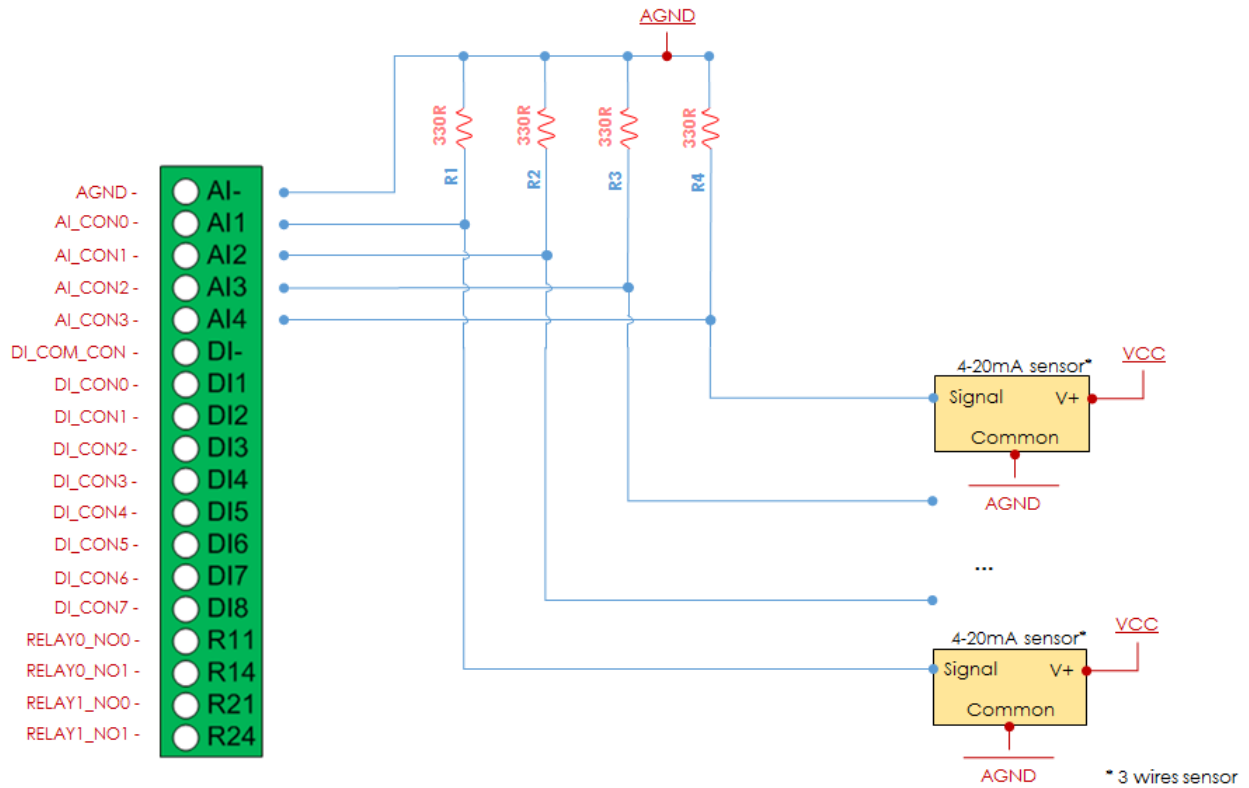

4. Converting 4-20mA signal into 0-10V

To connect your 4-20mA sensor to the FLX3401 extension card, perform the wiring as explained here above.

Using a resistor of 330 Ohm, you'll then need to specify inside the eWON Tag Setup page, a conversion factor of 20/43118.

Identification			
Tag Name:	AnalogInput1	Page:	Default
Tag Description:			
I/O Server Setup			
Server Name:	EWON	Topic Name:	
Address:	AI1	No Help	
Type:	Floating point	Force Read Only:	<input type="checkbox"/>
		eWON value = IO Server Value * 0.00046384 + 0	

The eWON Tag (AnalogInput1) will then reflect the 4-20mA input value.

If you need to apply supplementary conversion, simply add the conversion on top of the already existing one.

For example, let assume you have an 0-50 °C sensor. (4mA = 0°C, 20mA = 50°C).

You'll then need to apply following factor and offset inside the eWON Tag configuration:

Offset = -12.4

Factor = $3.125 * (20/43118) = 0.0014495$

Identification			
Tag Name:	AnalogInput1	Page:	Default ▼
Tag Description:			
I/O Server Setup			
Server Name:	EWON ▼	Topic Name:	▼
Address:	AI1		No Help
Type:	Floating point ▼	Force Read Only:	<input type="checkbox"/>
		eWON value = IO Server Value *	0.0014495 + -12.5

5. Explication of conversion and resistor values used

The following chapter explains why we suggest to use a resistor value of 330 Ohm.

5.1. AI (Analog Input) specifications of the FLX3401 extension card

The generic specifications of the FLX3401 extension card are:

- Precision = 16 bit
- Input range = 0 to 10V (absolute max. -0,6 to +12 VDC)
- Firmware coding: 0 to $2^{16}-1$ (65536 points)
- Over-voltage protected
- sampling rate 4sps
- Maximum gain error = 0,4% (= 262 points)
- Input impedance = 106k

5.2. 4-20mA usual specifications

The typical impedance of an 4-20mA Analog Input is 200 to 600R

So the typical output voltage of 4-20mA sensors are:

	200R	300R	500R	600R
4 mA	0,8V	1,2V	2V	2,4V
20 mA	3V	6V	10V	12V

5.3. Converting in current input

As the table here above indicates, with a resistor of 500R, all the voltage range of the Analog Voltage input is used (from 2V to 10V = 80%).

So the best suited resistor would be: 500R 0,5W.

At 20mA, 0,2W will then be dissipated in the resistor. (RI^2).

Small, low voltage and/or low power sensors are not always capable to have a 10V output at 20mA.

So it would be better to use a for example a 330R resistor to make the conversion. This will only use about 50 % of the whole voltage range. But this still represent more than 30,000 points due to the 16 bit ADC. Which is more than enough to control a sensor.

To avoid too much precision lost in the resistor, be careful to choose high precision resistors, for example with a tolerance of 0,1%.

Example: [330R 0.5W 0.1%](#)

5.4. Resistor correction

The resistor, which we will use inside the wiring for the 4-20mA conversion, will be added in parallel to the already existing 106K input impedance of the 0-10V Analog Input.

So during the factor and offset calculation for the eWON Tag value configuration fields, we need to take following global impedance into account:

Conversion resistor [Ω] (R)	Global Input impedance [Ω] $= 1 / (1/106000 + 1/R)$
300	299,15
330	328,98
500	497,65
600	596,62



Revision

Revision History

Revision Level	Date	Description
1.0	10/07/2015	Original Document
1.1	02/11/2015	General improvement

Document build number: 23

Note concerning the warranty and the rights of ownership:

The information contained in this document is subject to modification without notice. Check <http://wiki.ewon.biz> for the latest documents releases.

The vendor and the authors of this manual are not liable for the errors it may contain, nor for their eventual consequences.

No liability or warranty, explicit or implicit, is made concerning the quality, the accuracy and the correctness of the information contained in this document. In no case the manufacturer's responsibility could be called for direct, indirect, accidental or other damage occurring from any defect of the product or errors coming from this document.

The product names are mentioned in this manual for information purposes only. The trade marks and the product names or marks contained in this document are the property of their respective owners.

This document contains materials protected by the International Copyright Laws. All reproduction rights are reserved. No part of this handbook can be reproduced, transmitted or copied in any way without written consent from the manufacturer and/or the authors of this handbook.

eWON sa, Member of ACT'L Group